


# Current electricity

## 1 Basics of electricity


- Current - The rate of flow of charge
- Potential difference - Work done per unit charge

## 2 Current-voltage characteristics


### 2.1 Ohmic Conductor

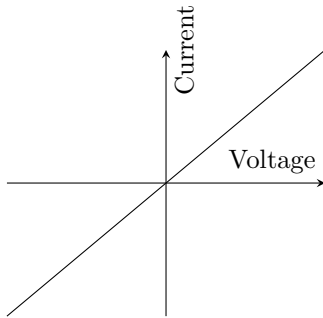

### 2.2 Bulb

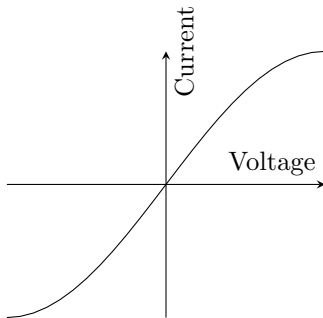


### 2.3 Diode

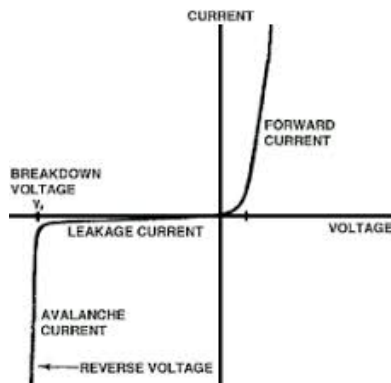

Ohm's Law: Current is proportional to voltage
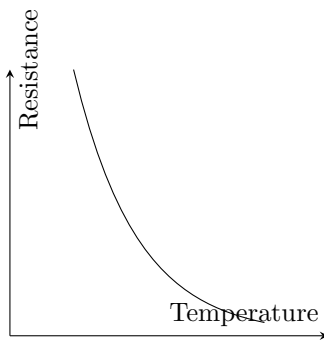
### 3 Resistivity

↓ Temperature ↓ Resistance of any conductor



### 4 Superconductivity

Below a certain temperature (critical temperature) the resistance of a material will be zero, this is described as superconductivity. The critical temperature depends on the material.

Applications:

- Producing strong magnetic fields
- The reduction in energy loss when transmitting power

### 5 Circuits

#### 5.1 Resistors

**Series:**  $R_T = R_1 + R_2 + R_3 \dots$

**Parallel:**  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$

#### 5.2 Current

**Series:** Current in = Current out. Current through multiple components is the same as through one

**Parallel:** Current into a junction = current out of a junction

#### 5.3 Voltage

**Series:** Total voltage = the sum of voltages in the circuit

**Parallel:** Voltage in parallel components is equal

### 6 Potential Dividers

A potential divider is used to supply constant or variable potential difference from a power supply

$$V_{Out} = V_{In} \frac{R_1}{R_1 + R_2}$$

Potential dividers can be used as part of sensor circuits to increase or decrease voltage based on environmental conditions

## 7 Electromotive force and internal resistance

|                            |                                 |
|----------------------------|---------------------------------|
| Switch Open                | Switch Closed                   |
| Voltmeter reads $\epsilon$ | Voltmeter reads $\epsilon - IR$ |

### 7.1 Voltage Current Graph

