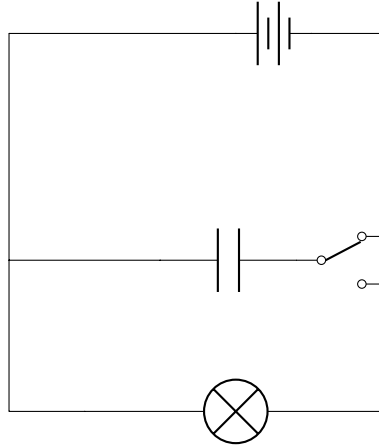


Capacitors

A capacitor is constructed from two conducting plates separated by an insulator. Charge can flow onto and off the plates but not across the plates.

1 Charging circuit for a capacitor




When charging the current flows round the top half of the circuit, when discharging the SPDT is changed to the other output and the current flows round the bottom half of the circuit.

Capacitors can be used as simple timers in circuits.

The time it takes to charge/discharge depends on:

- The capacitance of the capacitor (**C**)
- The resistance of the charging/discharging circuit (**R**)

2 Energy stored in a capacitor

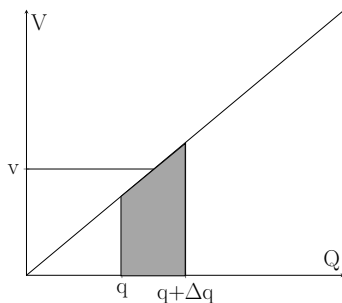

Area under graph=work done

v is the average P.D. as charge increases from q to $q + \Delta q$

$$\Delta w = v \Delta q$$

$$Q = \frac{1}{2} QV = E \text{ (Work done=energy stored)}$$

How to answer the exam question: Show that the energy stored by a capacitor is given by $E = \frac{1}{2} QV$

1. Sketch a graph of Q against V and describe what it shows
2. Describe that electrical energy is the product of charge and voltage
3. State QV is represented by the area under the line
4. The area under the line is a triangle with area $= \frac{1}{2} QV$

5. Therefore $E = \frac{1}{2}QV$

$$E = \frac{1}{2}QV$$

$$Q = CV$$


Therefore:

$$E = \frac{1}{2}CV^2$$

$$E = \frac{1}{2} \frac{Q^2}{C}$$

The battery supplies energy QV to the circuit but the capacitor only stores $\frac{1}{2}QV$, this means that 50% of the energy provided by the battery is wasted due to resistance in the circuit.

3 Charging and discharging a capacitor

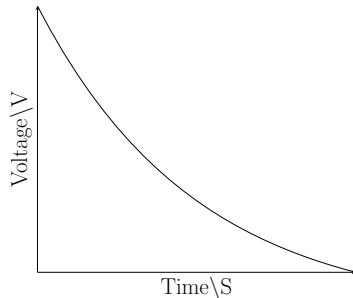

The smaller the resistor connected to the capacitor, the steeper the initial gradient

p.d. \propto rate of change of p.d.

Formula for discharge of a capacitor

$$Q = Q_0 e^{-\frac{t}{RC}}$$

Where:

Q =Charge at time, t

Q_0 =Initial charge

$e^{-\frac{t}{RC}}$ =Multiplication factor between 0 and 1

This also works for:

$$V = V_0 e^{-\frac{t}{RC}}$$

Formula for charging of a capacitor

$$Q = Q_0(1 - e^{-\frac{t}{RC}})$$

Rearranging for time

$$V = V_0 e^{-\frac{t}{RC}}$$

$$\frac{V}{V_0} = e^{-\frac{t}{RC}}$$

$$\ln\left(\frac{V}{V_0}\right) = -\frac{t}{RC}$$

$$t = -RC \ln\left(\frac{V}{V_0}\right)$$

$$t = RC \ln\left(\frac{V_0}{V}\right)$$

3.1 Proof of the units of the time constant being seconds

$$\tau = RC$$

$$\tau = \frac{V}{I} \times \frac{Q}{V} = \frac{Q}{I}$$

$$\frac{Q}{I} = t(\text{unit seconds})$$

4 Capacitor Discharge Theory

RC controls the rate of discharge

4.1 How much time remains after 1 time constant

$$Q = Q_0 e^{-\frac{t}{RC}}$$

$$Q = Q_0 e^{-\frac{RC}{RC}}$$

$$Q = Q_0 e^{-1}$$

e^{-1} is approximately 37%, this means that when charge is 37% of the initial value, 1 time constant will have passed.

4.2 Alternate way of finding the time constant

The x intercept of the graph of voltage against time if the initial gradient is continued is the time constant.

4.3 3rd method of finding the time constant

The formula $V = V_0 e^{-\frac{t}{RC}}$ can be rearranged to $RC = \frac{t}{\ln(\frac{V_0}{V})}$.

This means that using the initial voltage and the voltage at a point in time, the time constant can be calculated.

5 Dielectrics

Capacitance is increased by placing an insulator between the plates of a capacitor.

This means that more charge is stored on the capacitor for a given p.d. as:

- The positive side of the dielectric attracts more electrons from the supply
- The negative side of the dielectric pushes more electrons towards the supply

$$Q \propto C$$

6 Relative permittivity

This is the ratio of charge stored with the dielectric compared to the charge stored with no dielectric.

$$\epsilon_r = \frac{Q}{Q_0}$$

$$\epsilon_r = \frac{C}{C_0}$$

$$\epsilon = \epsilon_0 \epsilon_r$$

6.1 Capacitor design

$$C = \frac{A\epsilon_0\epsilon_r}{d} \text{ Therefore } C \propto A \quad C \propto \epsilon_r \quad C \propto \frac{1}{d}$$